

Note: Some K-Offset sensor require 5V or more and may require 5 to 100ma.


Bias resistor for flow sensor

VS = 35V, R1 = ~ 5.6k

VS = 12V, R1 = ~ 2k

VS = 5V, R1 = ~ 1k

VS = 3.3V, R1 = ~ 1k

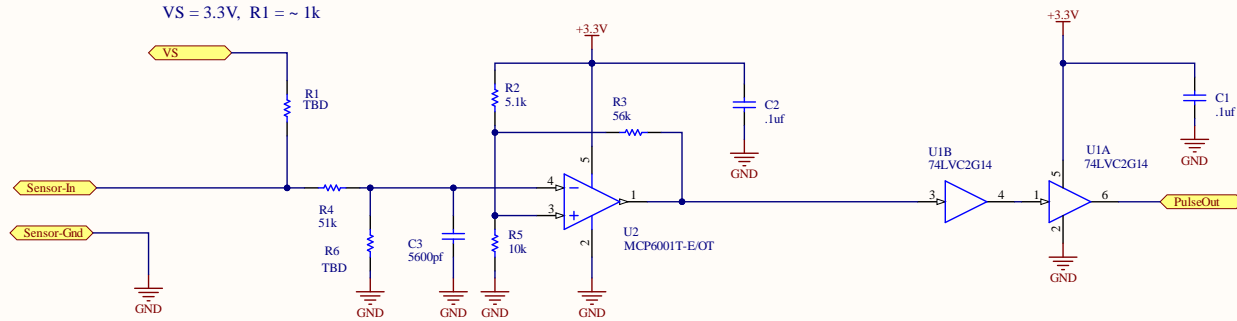

R6 maybe needed if VS is over 12V, 10-30k or so...